

Design1 - Multisim - [Design1 *]

File Edit View Place Simulate Transfer Tools Reports Options Window Help

Design Toolbox

Design1

Design1

Vin 10V

R1 5.6k Ω

R2 5.6k Ω

R3 50k Ω Key=A 50 %

Vout

XMM1

XMM2

XMM3

XMM4

XMM5

Multimeter-XMM1

982.79 μ A

Multimeter-XMM2

802.93 μ A

Multimeter-XMM4

179.856 μ A

Multimeter-XMM3

5.504 V

Multimeter-XMM5

4.496 V

Name: Sarkar Mehedi Hossain Rafi

ID:2533961043

Group:3

Multisim - Wednesday, 01 April 2026, 10:08:24 PM

Results Nets Components Copper layers Simulation