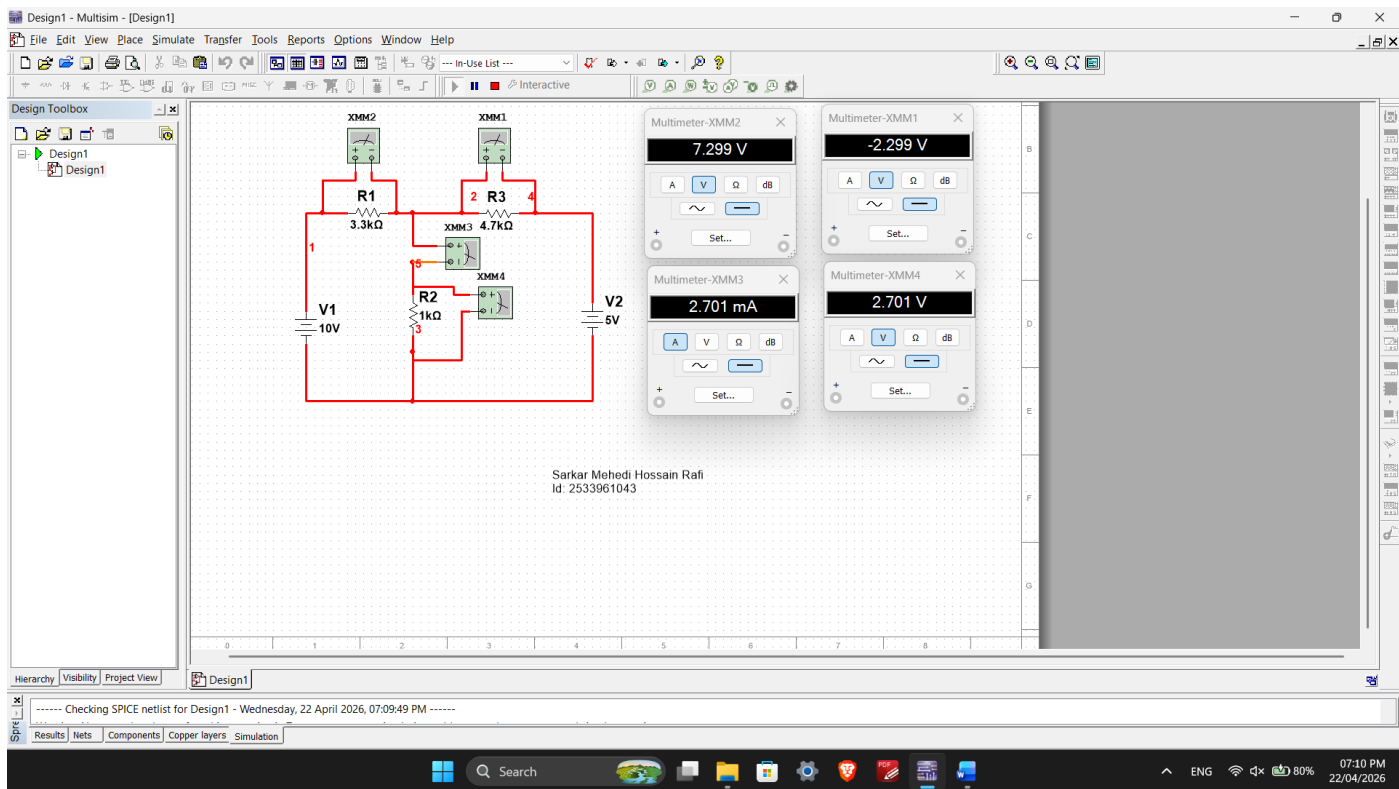
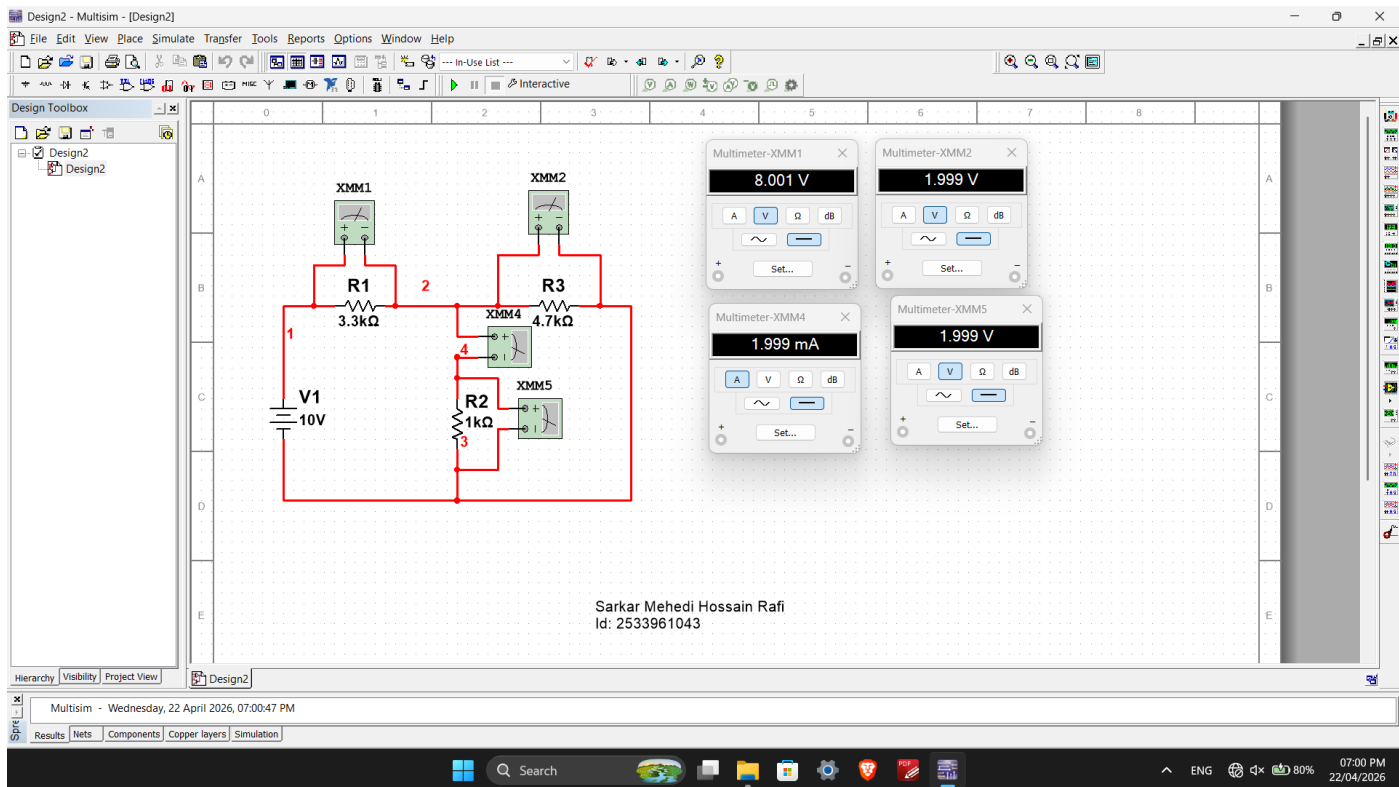




Sarkar Mehedi Hossain Rafi

Id: 2533961043



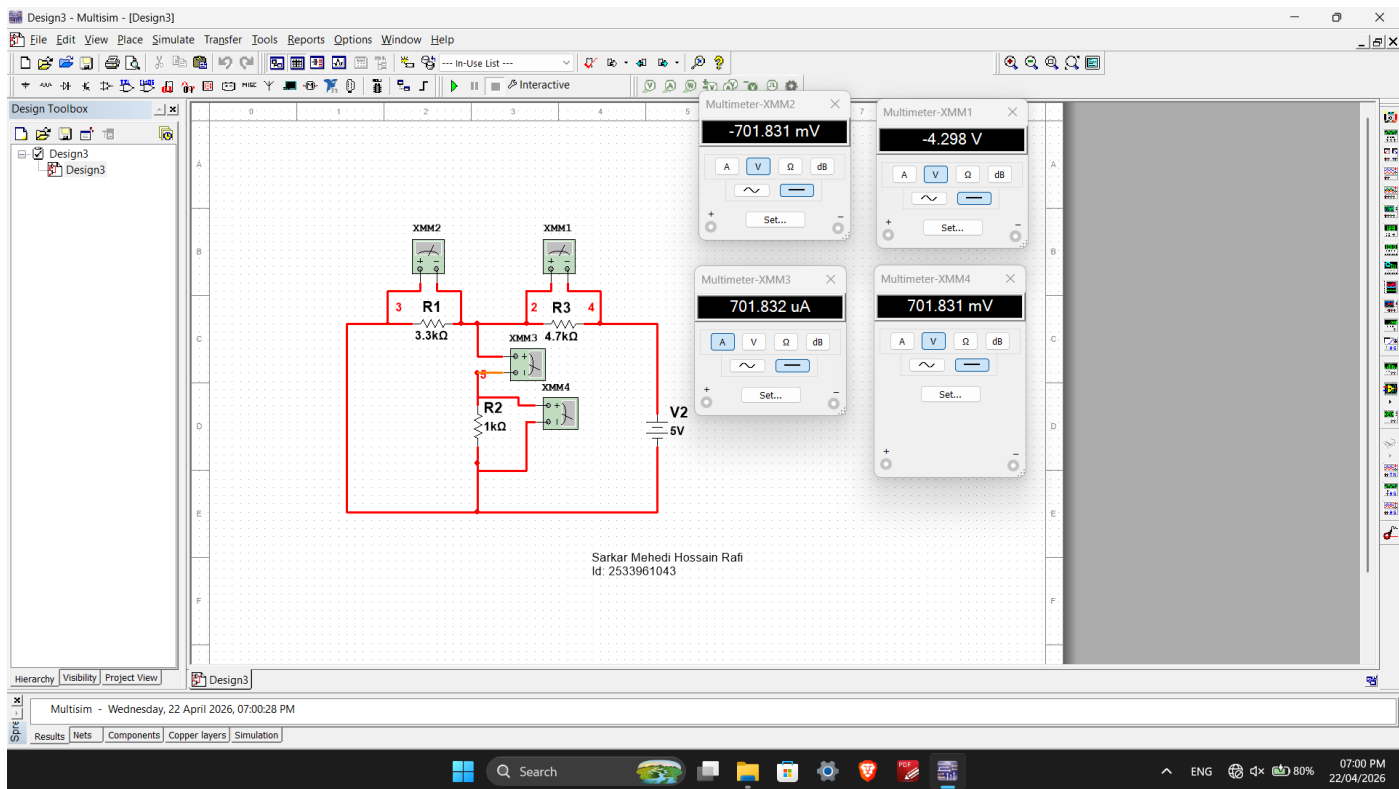


Table 1:

From Circuit 1	From Circuit 2	From Circuit 3	
I_{R2}	I'_{R2}	I''_{R2}	$I'_{R2} + I''_{R2}$
2.7A	2A	0.7A	2.7A

Table 2:

From Circuit 1	From Circuit 2	From Circuit 3	
V_{R1}	V'_{R1}	V''_{R1}	$V'_{R1} + V''_{R1}$
7.3V	8V	-0.7V	7.3V

Table 3:

From Circuit 1	From Circuit 2	From Circuit 3	
V_{R2}	V'_{R2}	V''_{R2}	$V'_{R2} + V''_{R2}$
2.7V	2V	0.7V	2.7V

Table 4:

From Circuit 1	From Circuit 2	From Circuit 3	
V_{R3}	V'_{R3}	V''_{R3}	$V'_{R3} + V''_{R3}$
-2.3V	2V	-4.3V	-2.3V