



Group No.:

Student Name:

Student ID:

Section: Date of Performance:

Signature

Construct the circuit shown in Figure S1 and complete the data table.

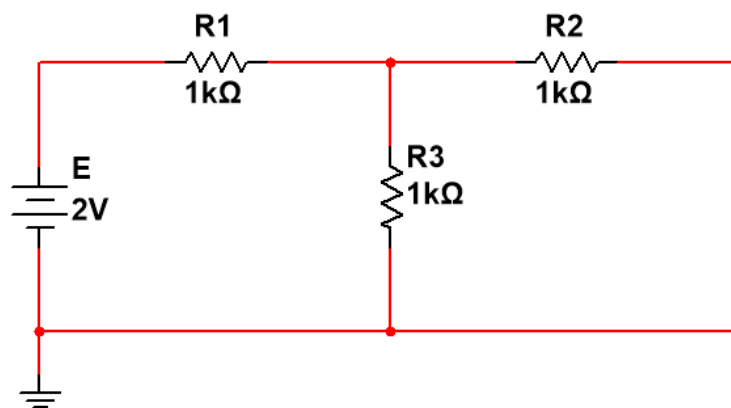


FIG. S1

Measurements	Theoretical	Practical	Percentage Error
Source Voltage, E	2V		
Resistance R_1	1k Ω		
Resistance R_2	1k Ω		
Resistance R_3	1k Ω		
Voltage across R_1	1.33V		
Voltage across R_2	666.67mV		
Voltage across R_3	666.67mV		
Source Current, I_s	1.33mA		



Group No.:

Student Name:

Student ID:

Section: Date of Performance:

Signature

Construct the circuit shown in Figure S2 and complete the data table.

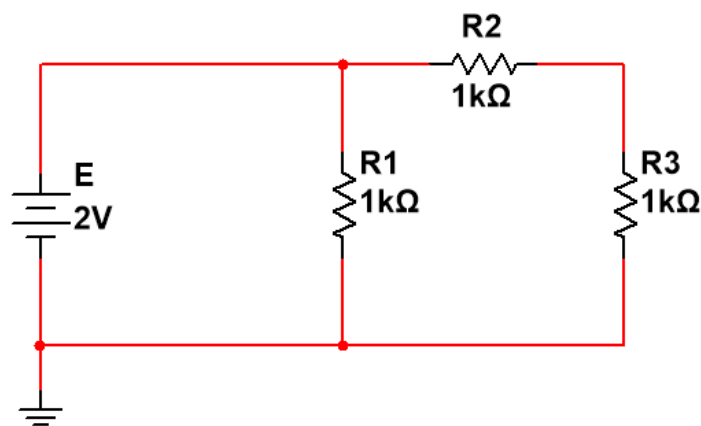


FIG. S2

Measurements	Theoretical	Practical	Percentage Error
Source Voltage, E	2V		
Resistance R ₁	1kΩ		
Resistance R ₂	1kΩ		
Resistance R ₃	1kΩ		
Voltage across R ₁	2V		
Voltage across R ₂	1V		
Voltage across R ₃	1V		
Source Current, I _S	3mA		



Group No.:

Student Name:

Student ID:

Section: Date of Performance:

Signature

Construct the circuit shown in Figure S3 and complete the data table.

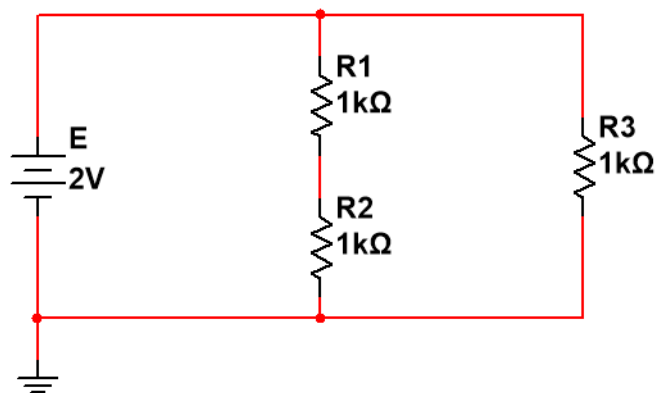


FIG. S3

Measurements	Theoretical	Practical	Percentage Error
Source Voltage, E	2V		
Resistance R ₁	1kΩ		
Resistance R ₂	1kΩ		
Resistance R ₃	1kΩ		
Voltage across R ₁	1V		
Voltage across R ₂	1V		
Voltage across R ₃	2V		
Source Current, I _S	3mA		



Group No.:

Student Name:

Student ID:

Section: Date of Performance:

Signature

Construct the circuit shown in Figure S4 and complete the data table.

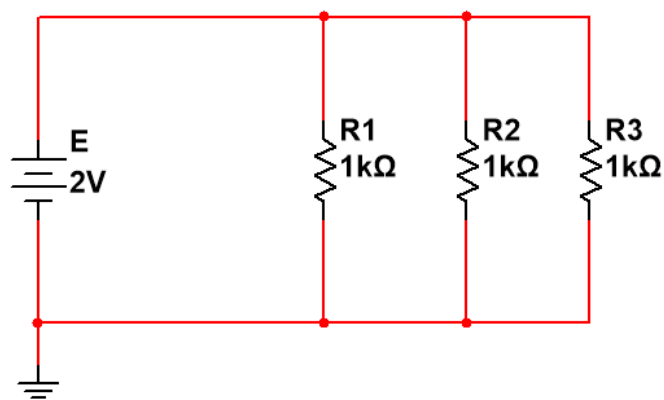


FIG. S4

Measurements	Theoretical	Practical	Percentage Error
Source Voltage, E	2V		
Resistance R ₁	1kΩ		
Resistance R ₂	1kΩ		
Resistance R ₃	1kΩ		
Voltage across R ₁	2V		
Voltage across R ₂	2V		
Voltage across R ₃	2V		
Source Current, I _s	6mA		