
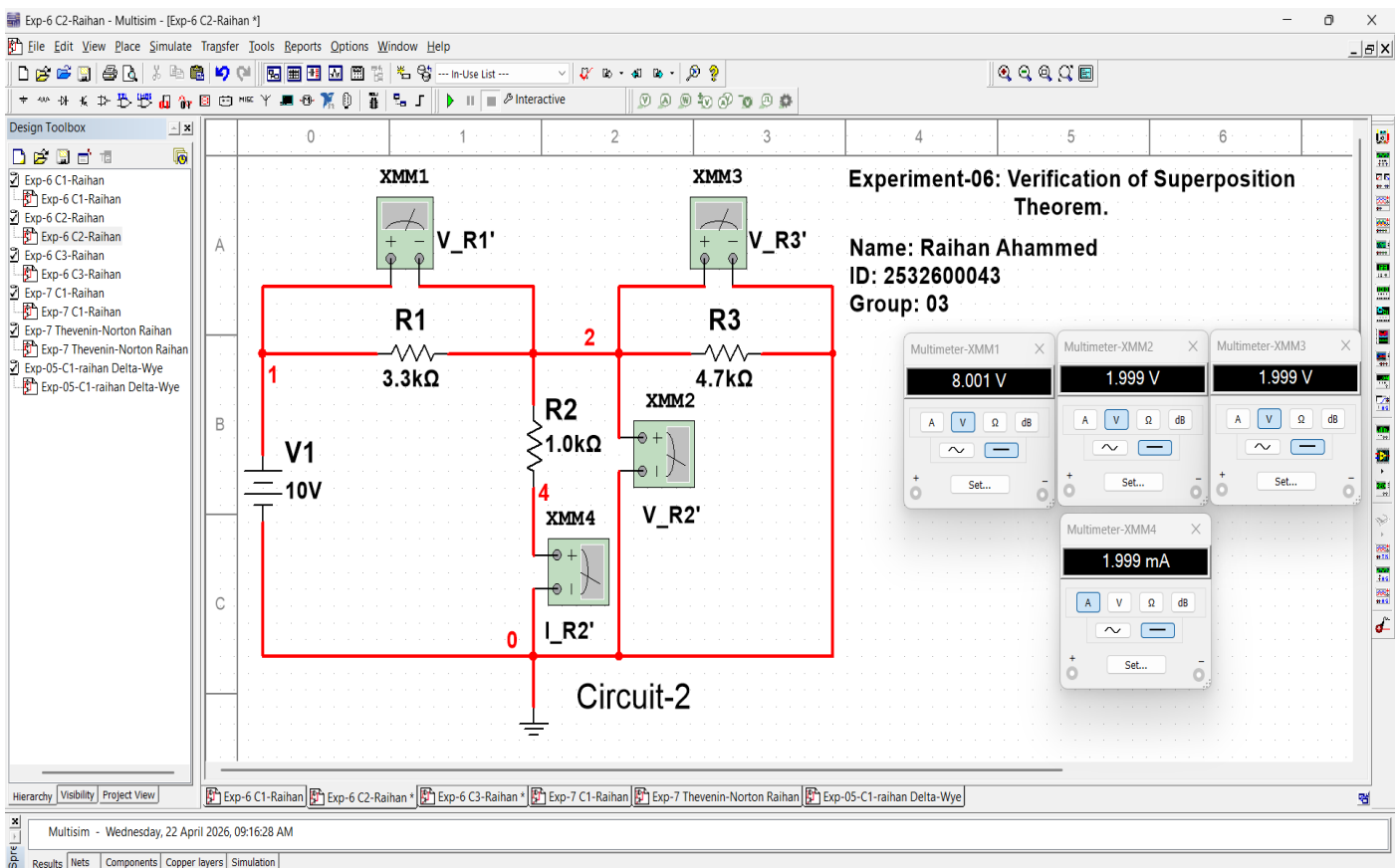


Experiment-06: Verification of Superposition Theorem

Name: Raihan Ahammed

ID: 2532600043

Group: 03

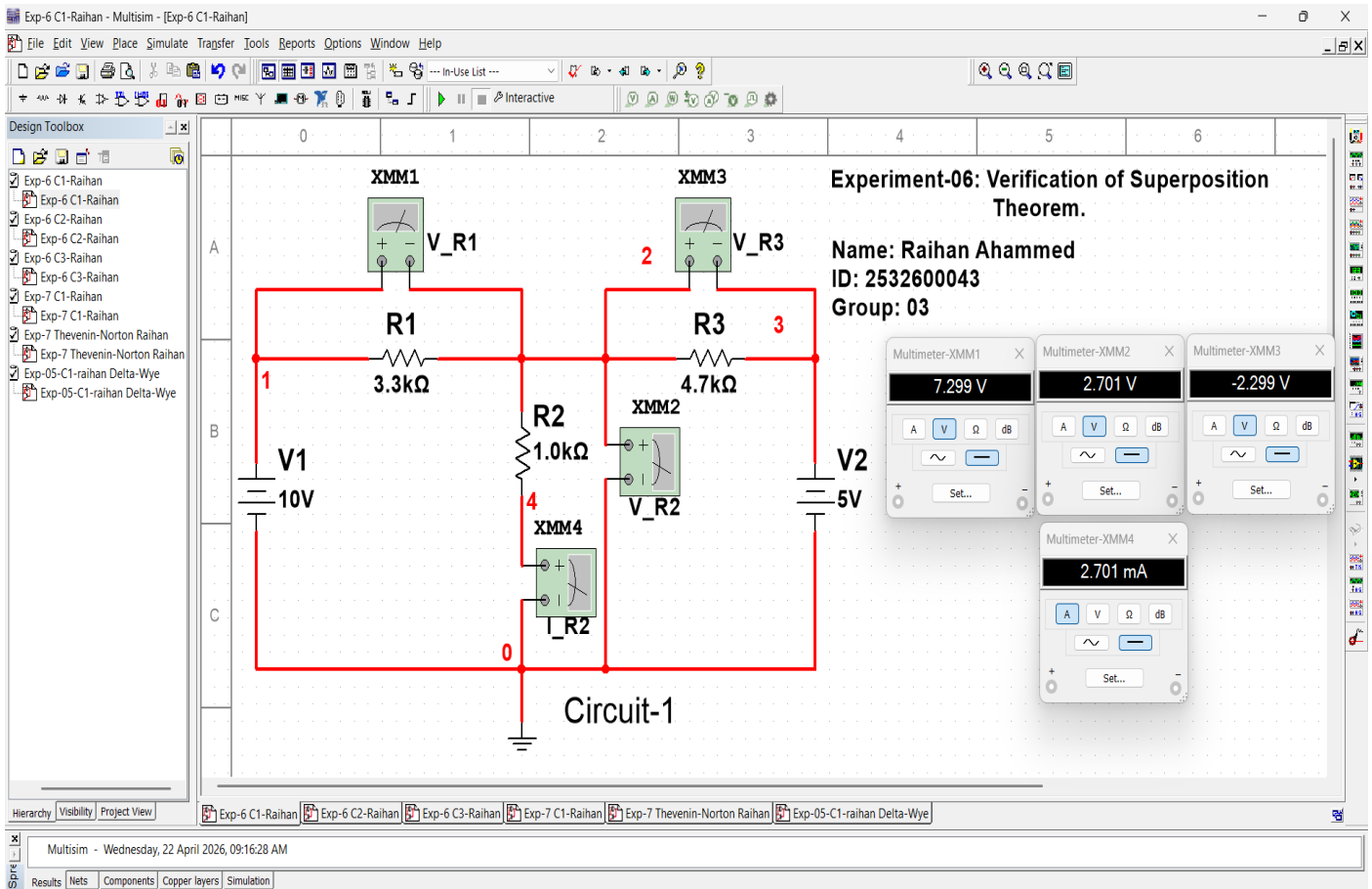

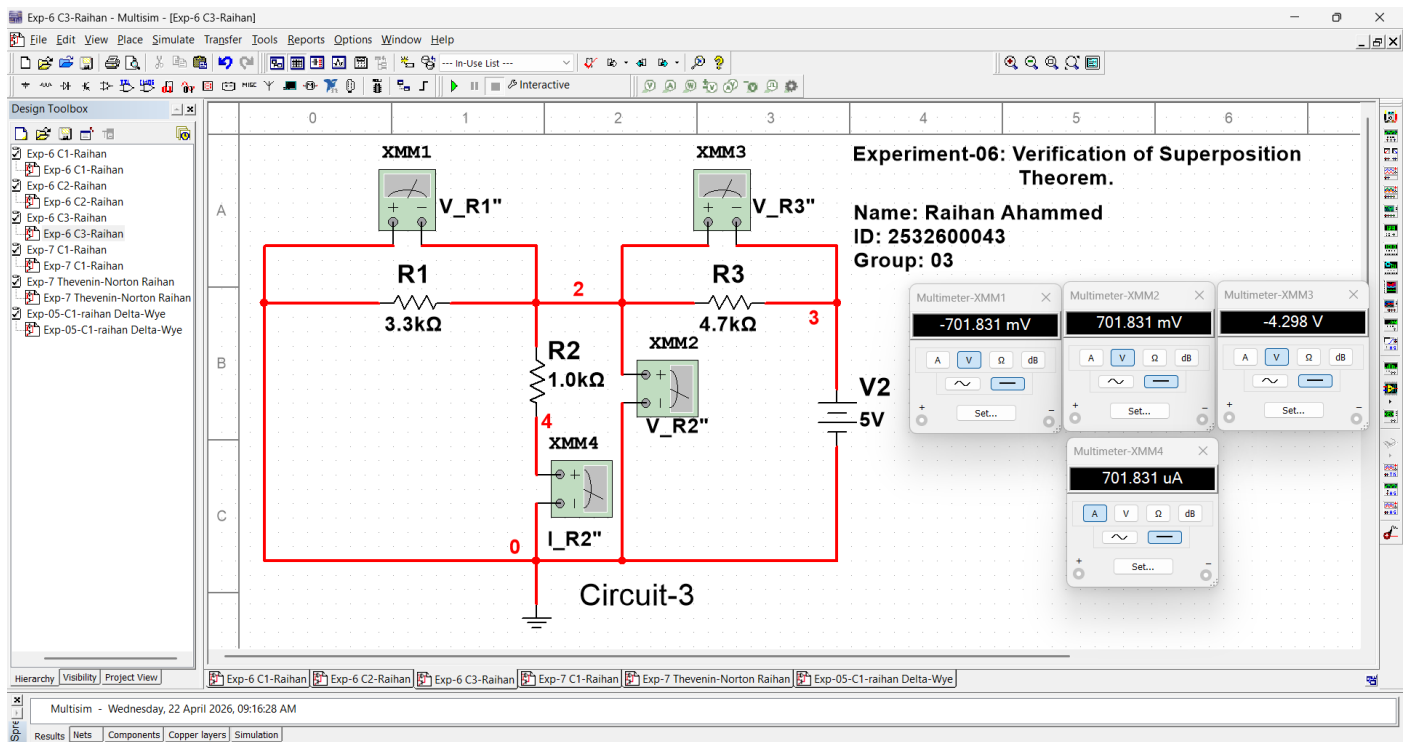


Table 1:

From Circuit 1	From Circuit 2	From Circuit 3	
IR2	I'R2	I''R2	I'R2 + I''R2
2.7A	2A	0.7A	2.7A

Table 2:

From Circuit 1	From Circuit 2	From Circuit 3	
VR1	V'R1	V''R1	V'R1 + V''R2
7.3V	8V	-0.7V	7.3V

Table 3:

From Circuit 1	From Circuit 2	From Circuit 3	
VR2	V'R2	V''R2	V'R2 + V''R2
2.7V	2V	0.7V	2.7V

Table 4:

From Circuit 1	From Circuit 2	From Circuit 3	
VR3	V'R3	V''R3	V'R3 + V''R3
-2.3V	2V	-4.3V	-2.3V