
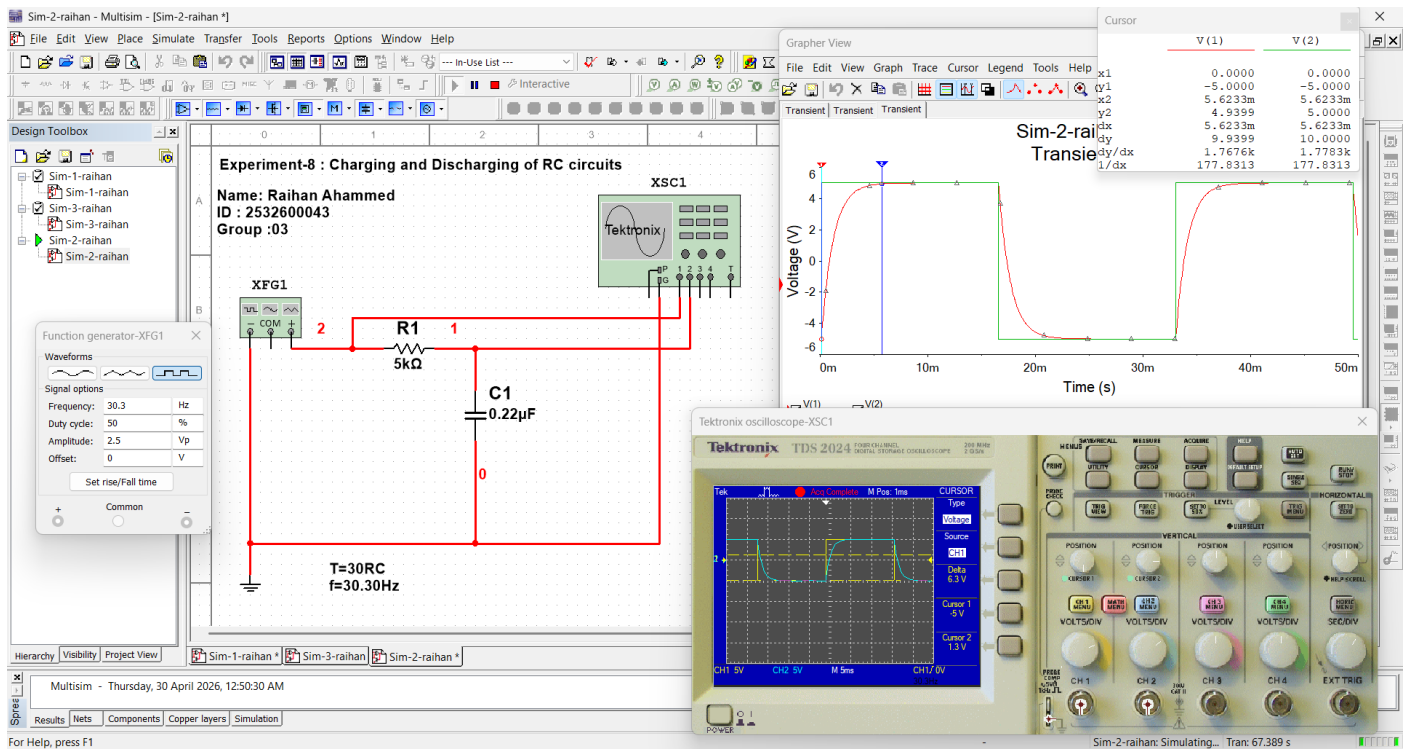


Experiment-08: Charging and Discharging of RC circuits

Name: Raihan Ahammed ID: 2532600043 Group: 03

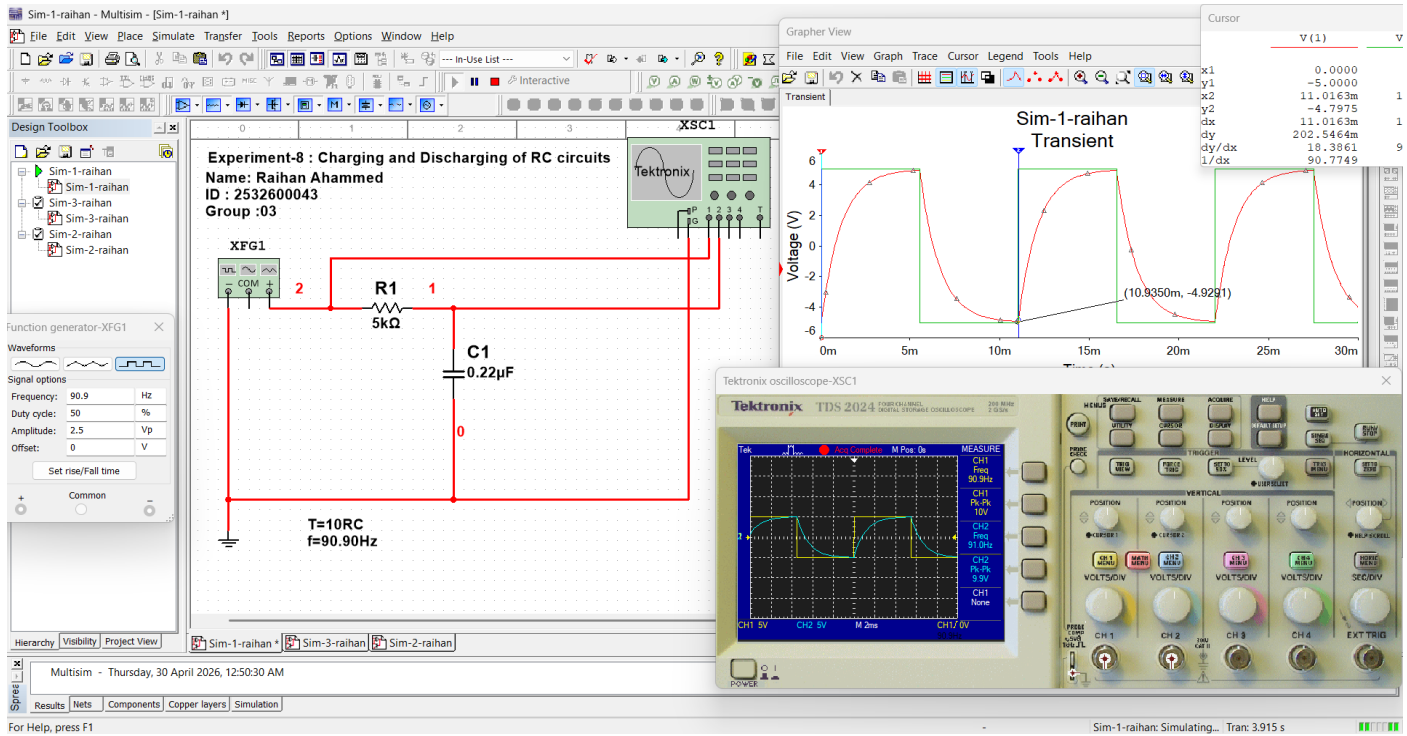

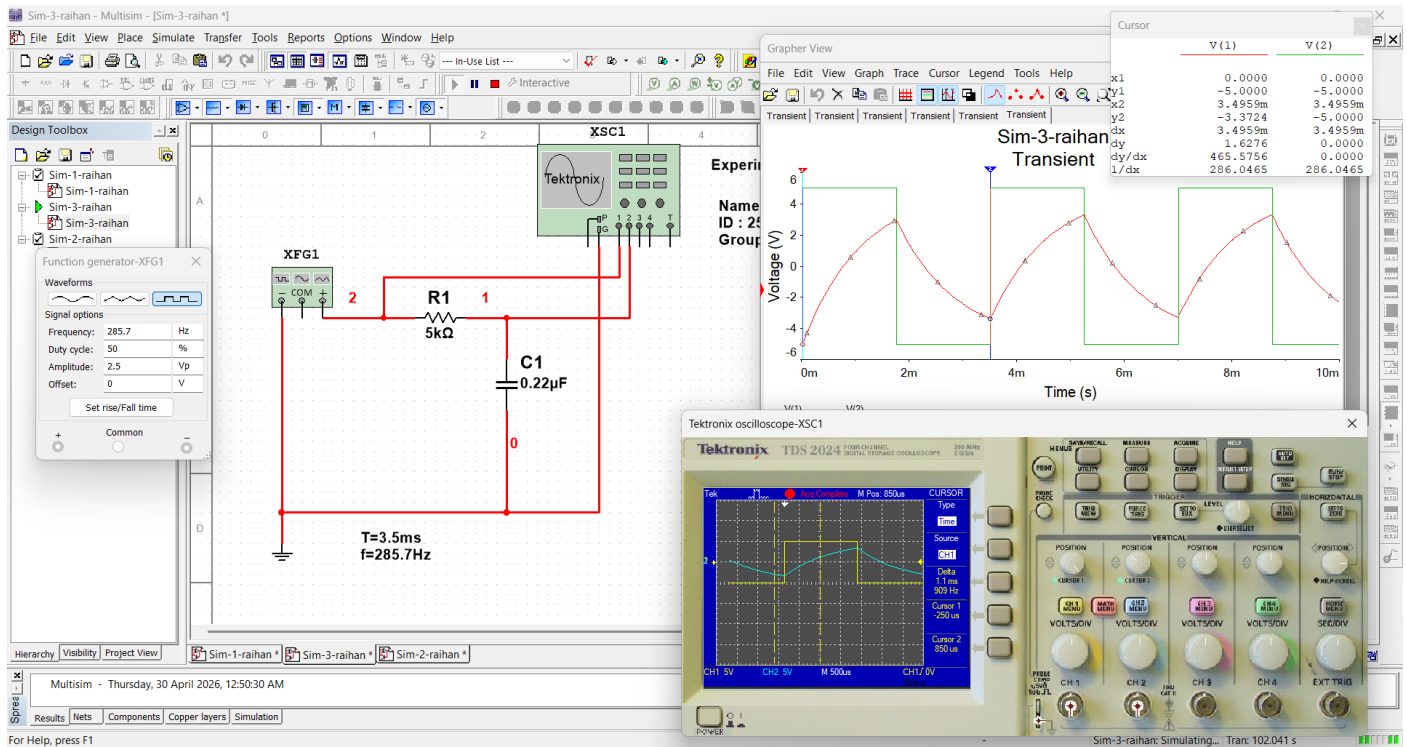


Table-1:

Measurement	$T=10RC$	$T=30RC$	$T=3.5ms$
Frequency of input signal	90.90Hz	30.30Hz	285.7Hz
Time constant, τ	1.16ms	1.17ms	1.13ms
Final Output V_c	9.9V(p-p)	10v(p-p)	6.67V(p-p)
Measure the time the capacitor charges up to V_c	5.54ms	5.4ms	1.76ms
Time the capacitor starts to discharge	5.54ms	16.3ms	1.76ms
Time the capacitor stops discharging	11ms	32.7ms	3.5ms